

## 12.2 DC Circuits

We define the following quantities on each element in a circuit.

- **Current**

$$I \equiv \frac{dQ}{dt}, \quad (12.47)$$

where  $Q$  is the charge that passes through a fixed cross section on the circuit.

The cross section is defined with the choice of a normal direction  $\hat{\mathbf{n}}$ , and the current is positive or negative if it flows in the  $\hat{\mathbf{n}}$  or  $(-\hat{\mathbf{n}})$  direction.

**Q 12.61:** As the current flows in a conducting wire in a DC circuit, what makes the field line bend to follow the wires?

We assume that, except on capacitors, there is no charge accumulation on a circuit, so that the current is everywhere the same regardless of how the cross-sectional surface is defined.


Just like how we have defined charge density  $\rho$ , surface charge density  $\sigma$ , and line charge density  $\lambda$  for the electric charge, for the electric current  $I$ , we define current density  $\mathbf{J}$ , and surface current density  $\mathbf{K}$ . The current density  $\mathbf{J}$  is the current per unit area, and the surface current density  $\mathbf{K}$  is the current per unit length.

**Q 12.62:** What is the current  $I$  along a strip of conductor of width  $L$  with a uniform surface current density  $K$ ?

There are actually small amount of charges accumulated at various places on a circuit.

- **Voltage**

The voltage across a circuit element is also defined with the choice of a direction. It is conventionally defined together with the current as follows (with the exception of batteries). We label the two endpoints of a circuit element by  $+$  and  $-$ . The voltage across the element is defined to be  $V = V(+) - V(-)$ , and the current is positive if it flows from the end labelled  $+$  to the end labelled  $-$ .

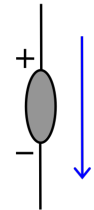

In the figure on the right, the arrow is used to define the reference direction. It does not have to agree with the actual direction of the current, as  $I$  can be both positive and negative. Similarly, the voltage of the point with the  $+$  sign is not necessarily higher than the point with the  $-$  sign.

- **Resistance**

$$R \equiv \frac{V}{I}. \quad (12.48)$$

- **Ohm's Law**

$R$  is (often, roughly) approximately a constant in a certain range of voltage/current for a resistor. (There is almost no information in this statement

$R$  is normally positive for resistors if we define  $V$  and  $I$  in the way described above.

except that it appears to hold in all experiments people have done during Ohm's time.)

- **Resistivity**

The *resistivity* (which is unfortunately also conventionally denoted as  $\rho$ ) of a material is defined by  $\rho \equiv RA/\ell$ , where  $R$  is the resistance of the resistor made of this material as a tube of length  $\ell$  and cross-sectional area  $A$ .

**Q 12.63:** Why is  $\rho$  expected to be independent of  $A$  and  $\ell$ ?

- **Power**

$$P \equiv \frac{dE}{dt} = IV, \quad (12.49)$$

where  $E$  is the energy dissipated over an element.

- **DC  $\equiv$  Direct Current, AC  $\equiv$  Alternating Current.**

We will first discuss DC circuits.

It refers to the source of electric power.

- **Kirchhoff's Rules:**

**Kirchhoff's Junction Rule:**  $\sum_i I_i = 0$ .

**Kirchhoff's Loop Rule:**  $\sum_a V_a = 0$ .

**Q 12.64:** Why do Kirchhoff's laws hold?

The assumptions behind Kirchhoff's laws are that there is no time-dependent net charges accumulated anywhere on the circuits and that there is no time-dependent magnetic field passing through the circuit.

- **Series And Parallel Connections**

Two elements in series have the same current; two elements in parallel have the same voltage.

**Superposition Principle**


The circuit elements  $R$ ,  $C$ ,  $L$  are linear elements, because when the current  $I_1(t)$  is associated with the potential  $V_1(t)$ , and  $I_2(t)$  with  $V_2(t)$ , we immediately know that the current  $I(t) = aI_1(t) + bI_2(t)$  is associated with the potential  $V(t) = aV_1(t) + bV_2(t)$ .

The Kirchhoff's rules are linear. Hence, a circuit with only linear elements obey superposition principle.


The batteries are not linear because its voltage is a fixed number. But we can imagine superposing a battery  $V_1$  with another battery  $V_2$  to obtain a new battery  $V = V_1 + V_2$ .

A conducting wire is the same as a battery with  $V = 0$ .

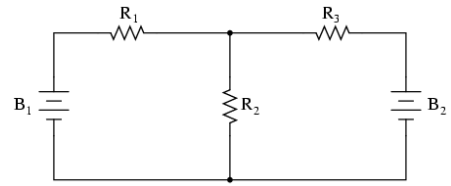**Ex 12.45:** Find the current on the resistors for (1)  $V_{B_1} = V_1$  and  $V_{B_2} = 0$ , and (2)  $V_{B_1} = 0$  and  $V_{B_2} = V_2$ . Show that the current on the resistors is a superposition of these two problems when  $V_{B_1} = V_1$  and  $V_{B_2} = V_2$ .




## 12.2.1 RC Circuits

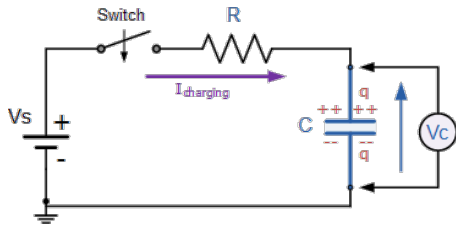

**Ex 12.46:** For the circuit above, if the circuit is closed at  $t = 0$ , and the capacitor has a constant voltage  $V_0$  for  $t < 0$ , what is the voltage on the capacitor  $V_C(t)$  for  $t > 0$ ? (The resistance of the resistor is  $R$  and the battery has a constant voltage  $V_S$ .)

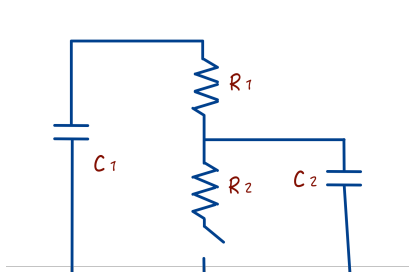**HW:** (2-3) See the figure below. For  $t < 0$ , the voltage across  $C_1$  is a given number  $V_1$ . The circuit is closed at  $t = 0$ . Find the voltage  $V(t)$  across  $C_1$  for  $t > 0$ . For simplicity, let  $C_1 = C_2 = C$  and  $R_1 = R_2 = R$ .



Define  $V(t)$  such that it is positive when the upper plate of  $C_1$  has a higher voltage than the lower plate.

